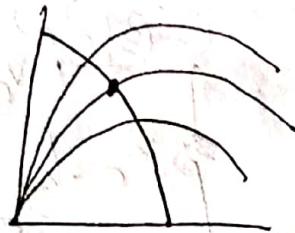


# Transistor Biasing

01.05.2020

27



Parameter variation

$$\alpha = 0.98 / 0.99$$


$$\beta = 49 / 99$$

$$T \uparrow I_{CBO} \uparrow I_c \uparrow T$$

stability factor,  $S = \frac{\delta I_c}{\delta I_{CBO}}$

6 375 मि circuit  
current २८

# Fixed biasing circuit

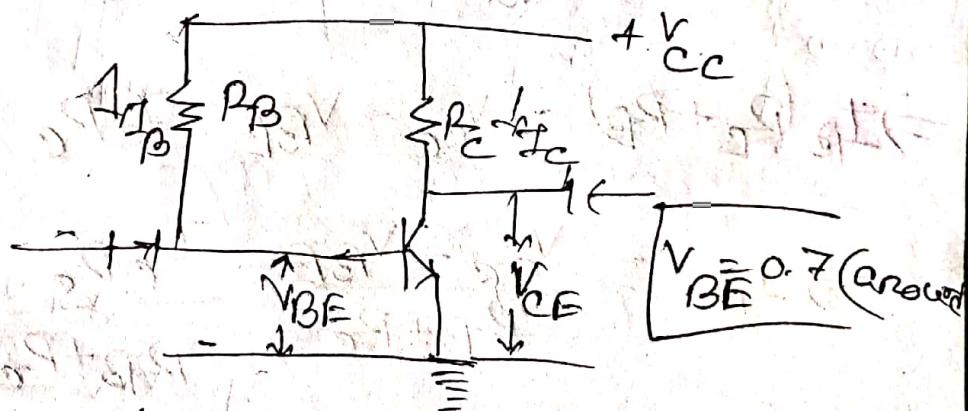

capacitance impedance

$$Z_C = \frac{1}{2\pi f C}$$

$$V_{CC} = I_B R_B + V_{BE}$$

$$I_B = \frac{V_C - V_{BE}}{R_B}$$

We know,

$$I_C = \beta I_B + (1+\beta) I_{CBO}$$


$$\Rightarrow \frac{\delta I_C}{\delta I_{CBO}} = \frac{\beta \left( \frac{V_C - V_{BE}}{R_B} \right) + (1+\beta) I_{CBO}}{I_{CBO}}$$

$$I_c = \beta I_B + (1+\beta) I_{CB0}$$

$I_{CB0} \rightarrow I_B + I_c$  28  
stability  
bias

Collector to base

$$V_{CE} = V_{BE} + I_B R_B - i)$$

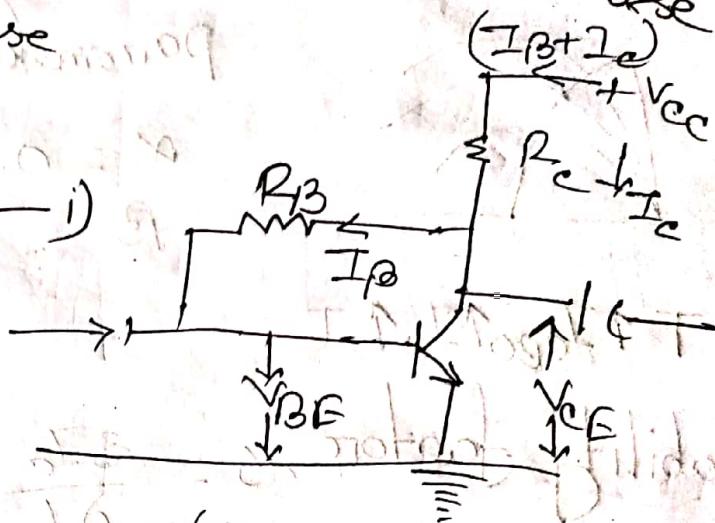

$$(I_B + I_c) R_c + V_E = V_{CC}$$

$$(I_B + I_c) R_c + V_{BE} + I_B R_B = V_{CC}$$

$$\Rightarrow I_B (R_c + R_B) = V_{CC} - V_{BE} - I_c R_c$$

$$\Rightarrow I_B = \frac{V_{CC} - V_{BE}}{R_B + R_c} - \frac{I_c R_c}{R_B + R_c}$$

We know,

$$I_c = \beta I_B + (1+\beta) I_{CB0}$$

$$I_c = \beta \left( \frac{V_{CC} - V_{BE}}{R_B + R_c} - \frac{I_c R_c}{R_B + R_c} \right) + (1+\beta) I_{CB0}$$

$$\Rightarrow I_c \left( 1 + \frac{\beta R_c}{R_B + R_c} \right) = \beta \cdot \frac{V_{CC} - V_{BE}}{R_B + R_c} + (1+\beta) I_{CB0}$$

if one side of semiconductor

if one side of a single crystal is doped

$$I_a = I_{a0} e^{-\frac{V_T}{kT_B} \ln \left( \frac{N_1 N_2}{n_1 n_2} \right)} = I_{a0} e^{-\frac{V_T}{kT_B} \ln \left( \frac{N_1 N_2}{n_1 n_2} \right)}$$

$$\Rightarrow \frac{\delta I_c}{\delta I_{CB0}} \left( 1 + \frac{\beta R_C}{R_B + R_C} \right) = 1 + \beta$$

$$\Rightarrow S = \frac{\delta I_c}{\delta I_{CB0}} = \frac{1 + \beta}{1 + \beta R_C / R_B}$$

$$S = \frac{1 + \beta}{1 + \frac{\beta R_C}{R_B}}$$

if  $R_B \ll R_C$


$$R_B / R_C \ll 1$$

$$S = \frac{1 + \beta}{1 + \beta} \approx 1$$

stability  $\pi_{13}(2)$  circuit poor

stability  $\pi_{13}(3)$  circuit clear

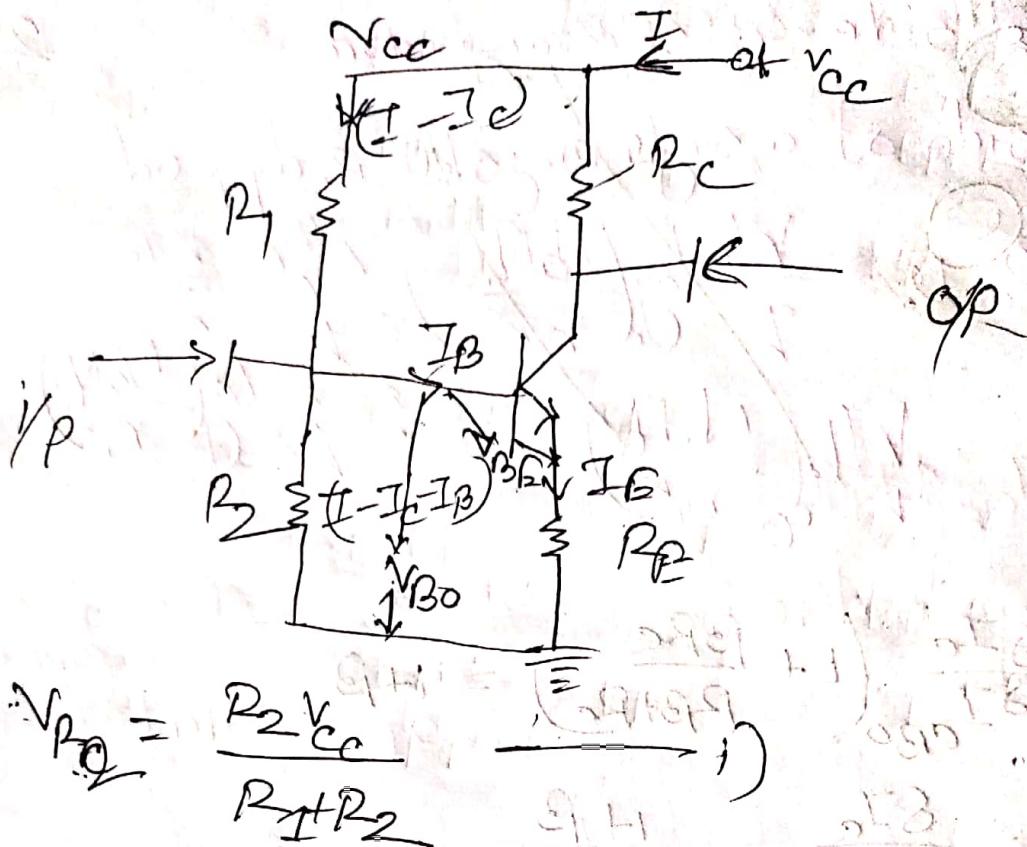If potential divider bias or ammeter bias:



$$V_{BO} = V_{BE} + I_E R_E$$

$$\Rightarrow V_{BE} = V_{BO} - I_E R_E \quad \text{(ii)}$$

$$V_{BO} = (I - I_c - I_B) R_2$$

$$= (I - I_c) R_2 - I_B R_2 \quad \text{(iii)}$$

$$V_{CC} = (I - I_c) R_1 + (I - I_c - I_B) R_2$$

$$V_{CC} + I_B R_2 = (I - I_c)(R_1 + R_2)$$

$$\Rightarrow I - I_c = \frac{V_{CC} + I_B R_2}{R_1 + R_2} \quad \text{(iv)}$$

31

iii)  $\Rightarrow$ 

$$V_{BO} = \frac{V_{CC} + I_B R_2}{R_1 + R_2} R_2 - I_B R_2$$

$$= \frac{V_{CC} R_2 + I_B R_2^2 - I_B R_1 R_2 - I_B R_2^2}{R_1 + R_2}$$

$$V_{BO} = \frac{(V_{CC} - I_B R_1) R_2}{R_1 + R_2}$$

$$V_{BO} = \frac{V_{CC} R_2}{R_1 + R_2} - \frac{I_B R_1 R_2}{R_1 + R_2} \rightarrow$$

ii)  $\Rightarrow$ 

$$V_{BE} = \frac{V_{CC} R_C}{R_1 + R_2} - \frac{I_B R_1 R_2}{R_1 + R_2} + I_E R_E$$

$$\Rightarrow V_{BE} = \frac{V_{CC} R_C}{R_1 + R_2} - I_B \frac{R_1 R_2}{R_1 + R_2} - I_C R_E - I_B R_E$$

$\left[ \because I_E = I_C + I_B \right]$

$$\Rightarrow V_{BE} = \frac{V_{CC} R_C}{R_1 + R_2} + I_C R_E - I_B \left( \frac{R_1 R_2}{R_1 + R_2} + R_E \right)$$

$$\Rightarrow I_B = \frac{\frac{V_{CC} R_C}{R_1 + R_2} - V_{BE} - I_C R_E}{\left( \frac{R_1 R_2}{R_1 + R_2} + R_E \right)}$$

$$\Rightarrow I_B = \frac{V_{CC} R_2}{R_1 + R_2} - \frac{V_{BE}}{\frac{R_1 R_2}{R_1 + R_2} + R_F} - \frac{I_C R_E}{\frac{R_1 R_2}{R_1 + R_2} + R_E} \quad 32$$

n)

$$\therefore I_C = I_B \beta + (1+\beta) I_{CBO}$$

$$\Rightarrow I_C = \beta \left[ \frac{V_{CC} R_2}{R_1 + R_2} - \frac{V_{BE}}{\frac{R_1 R_2}{R_1 + R_2} + R_F} - \frac{I_C R_E}{\frac{R_1 R_2}{R_1 + R_2} + R_E} \right] + (1+\beta) I_{CBO}$$

$$\Rightarrow I_C \left( 1 + \beta \cdot \frac{R_E}{\frac{R_1 R_2}{R_1 + R_2} + R_E} \right) = \beta \left( \frac{V_{CC} R_2}{R_1 + R_2} - V_{BE} \right) + (1+\beta) I_{CBO}$$

$$\Rightarrow \frac{\delta I_C}{\delta I_{CBO}} = \frac{1+\beta}{\frac{R_E}{\frac{R_1 R_2}{R_1 + R_2} + R_E}}$$

$$I_C = \beta \left( \frac{\frac{V_{CC}R_2}{R_1+R_2} - V_{BE} - I_C R_E}{\left( \frac{R_1 R_2}{R_1+R_2} + R_E \right)} \right) \quad 3.3$$

$+ (1+\beta)$   
 $I_{CBO}$

$$= \beta \left( \frac{V_C}{R_E + \frac{R_1 R_2}{R_1+R_2}} \right)$$

$$\frac{\delta I_C}{I_{CBO}} = \frac{R_E + \frac{R_1 R_2}{R_1+R_2}}{R_E + \left( \frac{1}{\beta+1} \right) \frac{R_1 R_2}{R_1+R_2}}$$

$[1+\beta = 51]$   
 $\frac{1}{1+\beta} = 0.02$

exam - 27.57mA - 20% wrt


Repet factor, full wave rectified.

05-01-2020


# Field Effect Transistor (FET) 34-

(910) 2.

cost

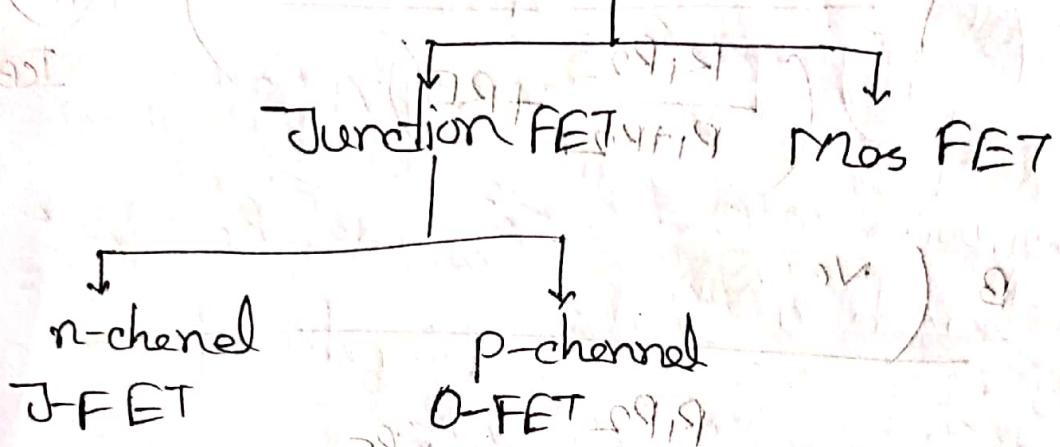


## # n-channel J-FET

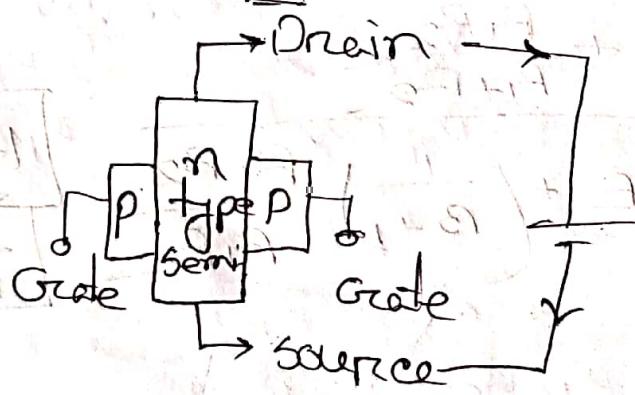


# channel doped  
lightly

# gate doped  
heavily

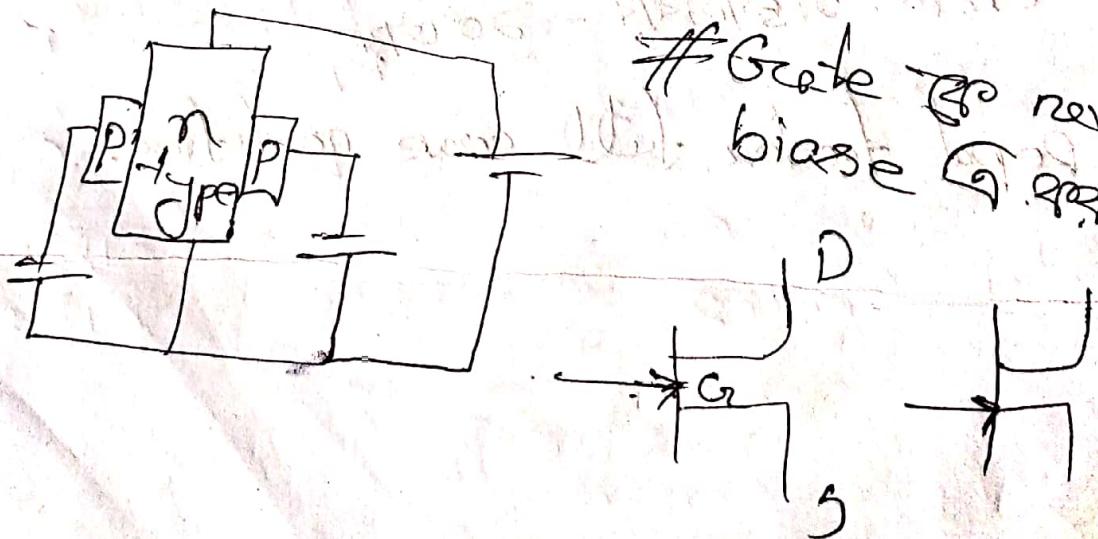


# Gate reverse biased


bias

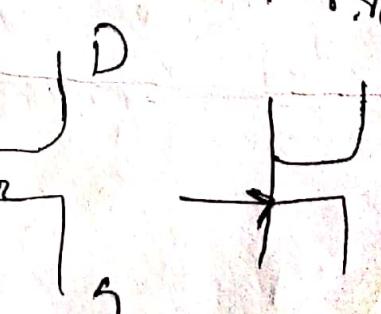


$V_A > V_B > V_C > V_D$

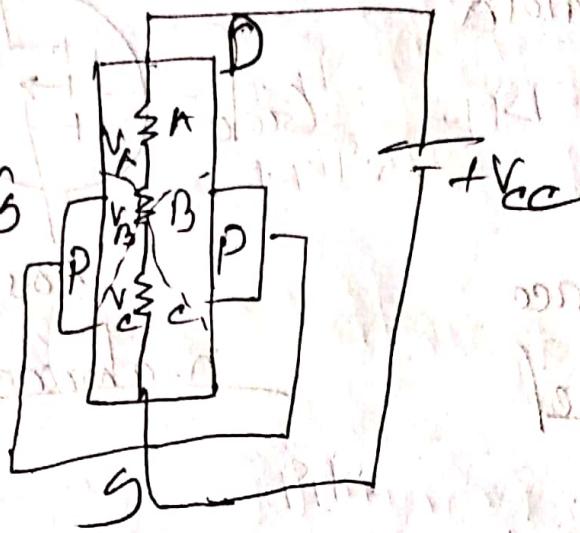

35

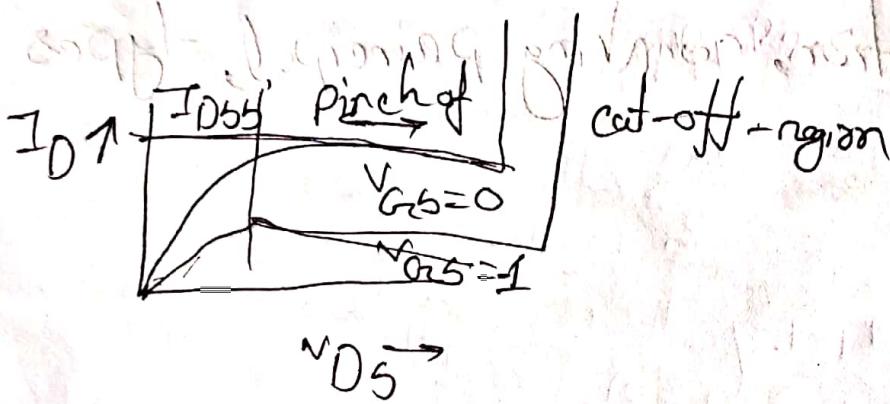



# Mosfet 2 types.

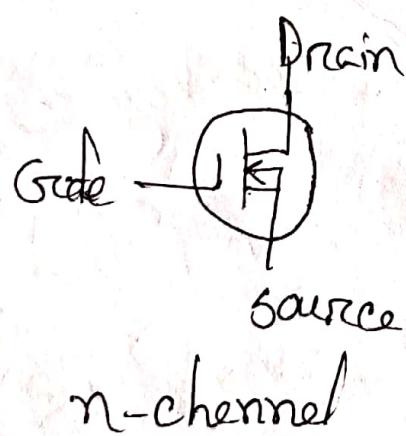

few voltage द्वारा उत्पन्न करने वाली वोटेज या  
pinch off voltage एवं,

# Enhancement-mode mosfet (E-mosfet)

## Symbol - of F-MosFET

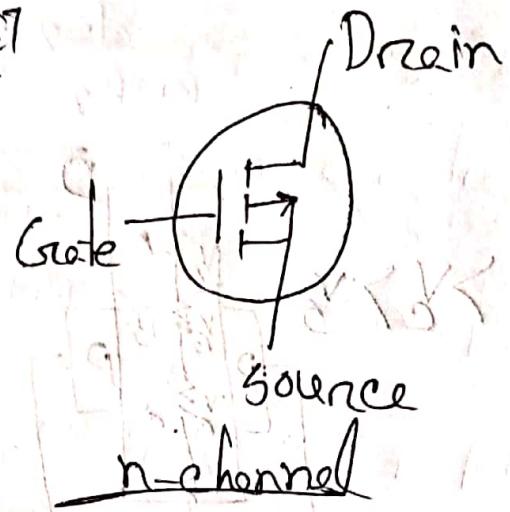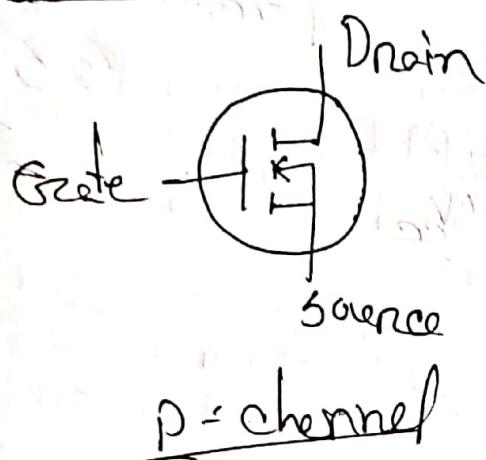

# Fet, classification, working principle, -types  
of fet, curve



curve

forward - N

reverse - P

forward - P

reverse - N

forward - N

reverse - P

forward - P

reverse - N

forward - N

reverse - P

forward - P

reverse - N

forward - N

reverse - P


forward - P

reverse - N

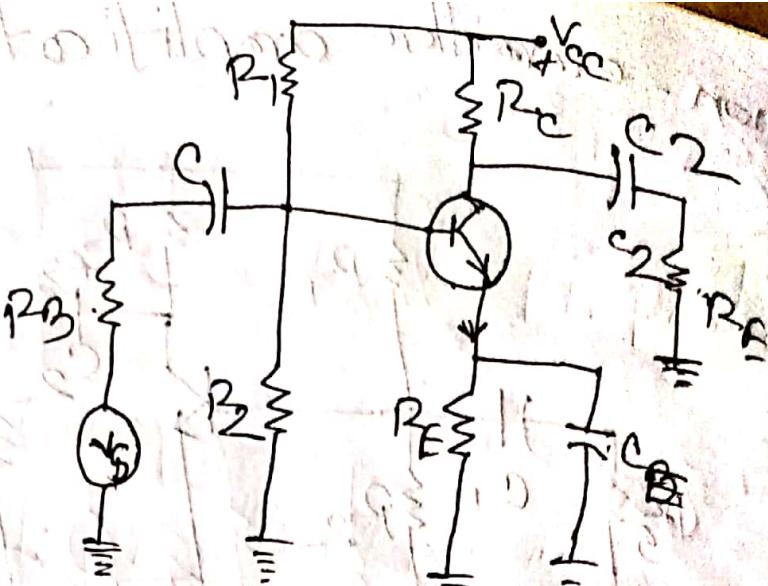

Common-emitter

# transistor amplifier.

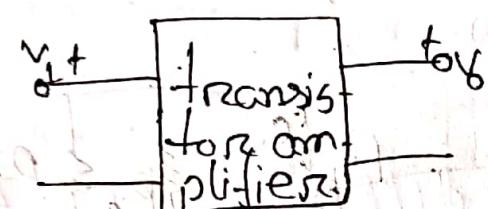

$$V_i = h_{11}I_i + h_{12}V_o \rightarrow \text{input}$$





$$I_o = h_{21}I_i + h_{22}V_o \rightarrow \text{output}$$

# Benefit of h-parameters.

# h-parameter for all three configuration

# Method for analysis of a transistor circuit

# common-emitter amplification

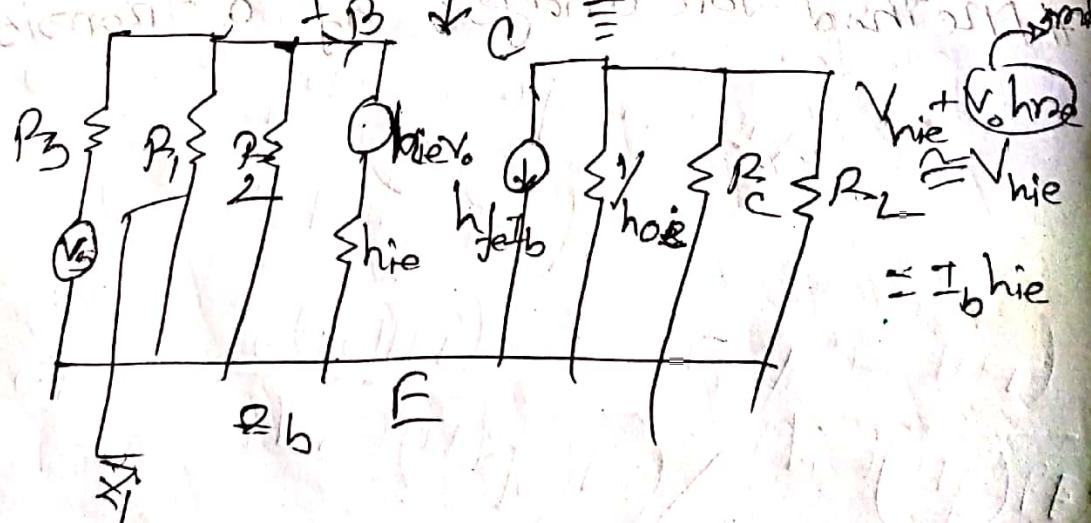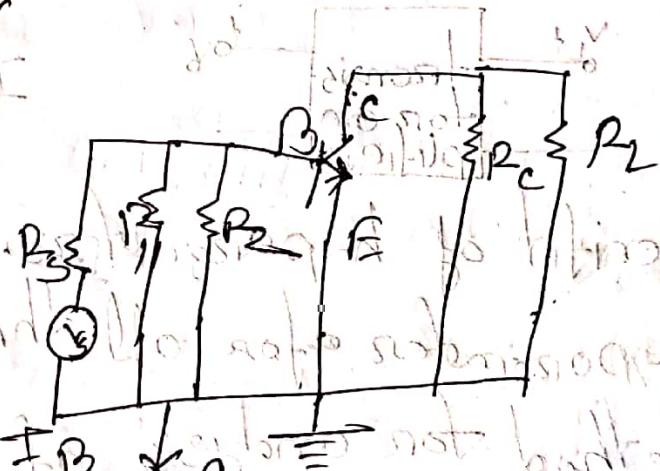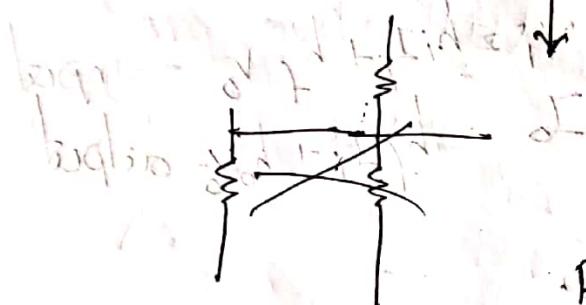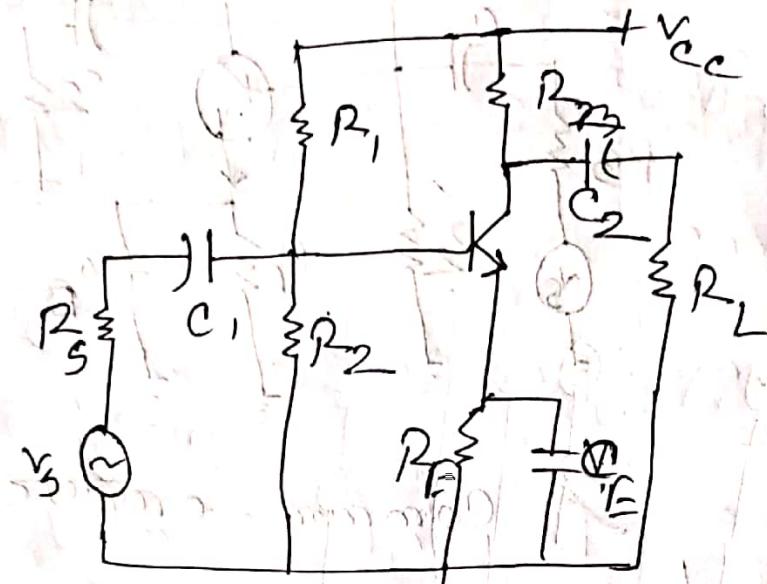


input impedance

$$Z_b = \frac{h_{ie} I_b}{I_b}$$

$$\approx h_{ie}$$

$$Z_b = R_1 || R_2 || R_{hie}$$

25μF capacitor at 2000

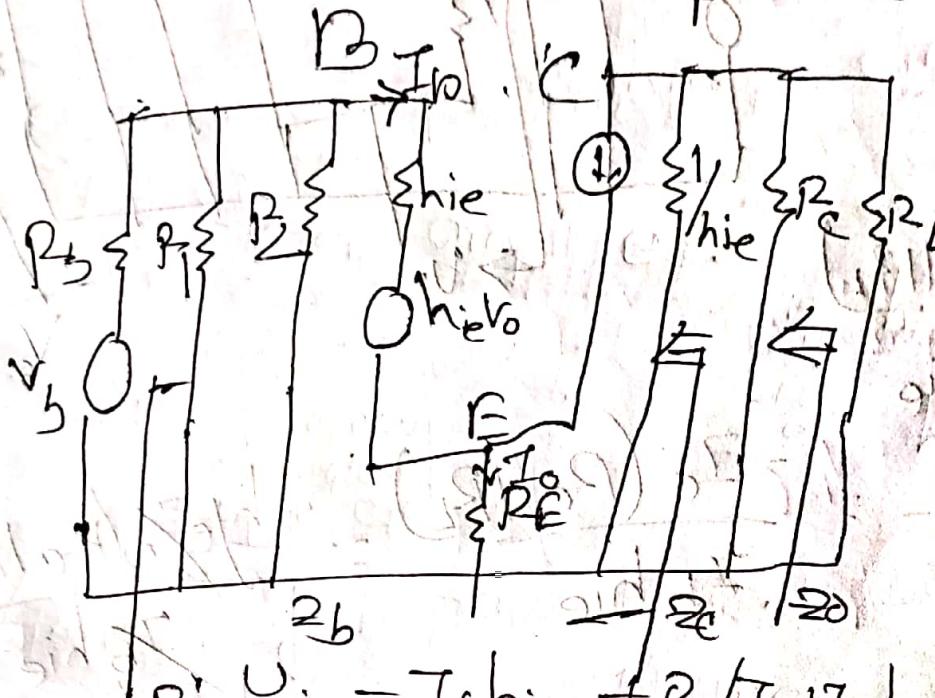

$$\frac{I_c}{I_b} = h_{fe}$$

$$V_i = I_b h_{ie} + R_E (I_b + I_c)$$

$$= I_b h_{ie} + R_E I_b + R_E h_{fe} I_b$$

$$V_i = I_b (h_{ie} + (1+h_{fe}) R_E)$$

$$\frac{V_i}{I_b} = \frac{(h_{ie} + (1+h_{fe}) R_E)}{R_b}$$

Output impedance

$$Z_C = \frac{1}{h_{oe}}$$

$$Z_o = Z_C || R_C$$

Current gain

Voltage gain


$$A_v = \frac{V_o}{V_i}$$

$$V_o = I_C (R_C || R_L)$$

$$V_i = I_b \cdot h_{ie}$$

$$A_v = \frac{V_o}{V_i} \Rightarrow \frac{-I_C (R_C || R_L)}{I_b \cdot h_{ie}} = -\frac{h_{fe} I_b (R_C || R_L)}{h_{ie}}$$

$$= +\frac{h_{fe} (R_C || R_L)}{h_{ie}}$$

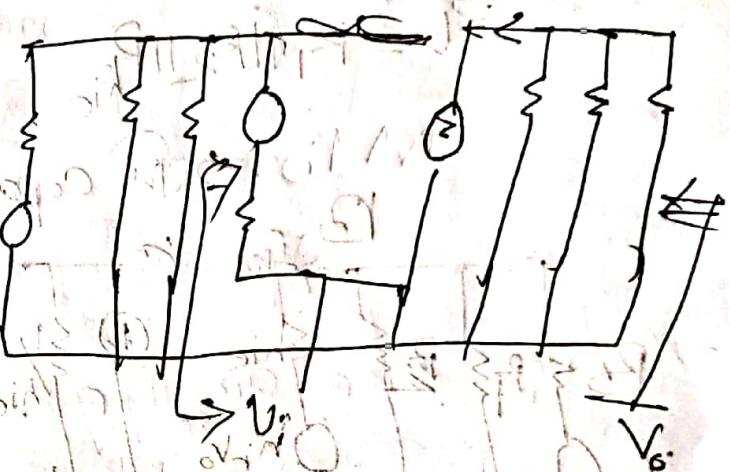

Voltage gain (capacitor at 27300 Hz)


$$i_{ei} = I_b (h_{ie} + (1+h_{fe}) R_E)$$

$$\therefore A_v = \frac{V_o}{V_i} = \frac{-I_C (R_C || R_L)}{I_b (h_{ie} + (1+h_{fe}) R_E)} = \frac{-h_{fe} I_b (R_C || R_L)}{I_b (h_{ie} + (1+h_{fe}) R_E)}$$

$$= \frac{-h_{fe}(R_C || R_L)}{(1+h_{fe})R_E}$$

if  $1+h_{fe} \gg h_{ie}$

$$\therefore A_{ve} = -\frac{R_C || R_L}{R_E} \quad 1+h_{fe} \approx \frac{99}{100}$$

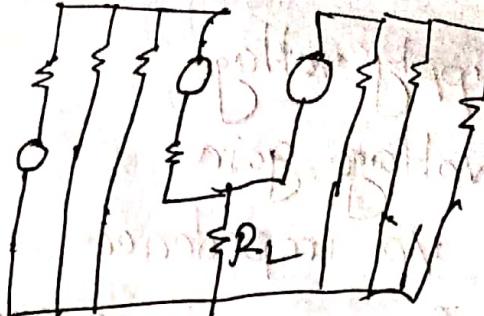

Current gain

$$h_{fe} = \frac{I_C}{I_B} \Rightarrow I_C = h_{fe} I_B$$


$$I_B = \frac{I_S \cdot R_B}{R_B + Z_B}$$

$$I_C = h_{fe} I_S R_B$$

$$\Rightarrow \frac{I_C}{I_S} = \frac{h_{fe} R_B}{R_B + Z_B}$$

$$I_L = \frac{I_C \cdot R_C}{R_C + R_L}$$
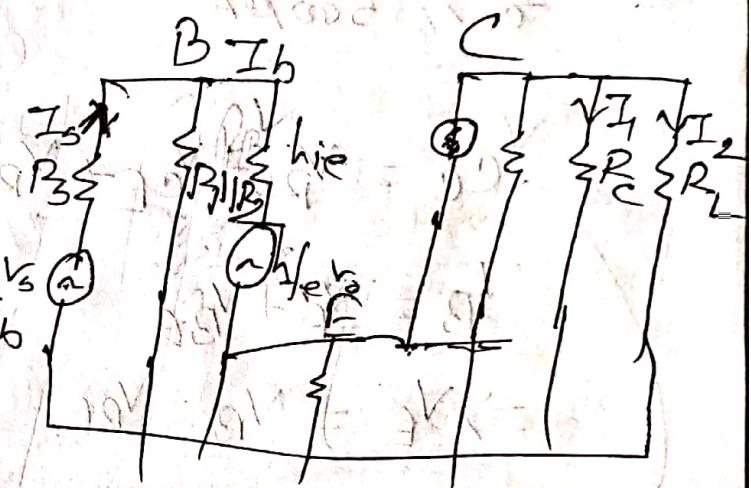
$$\Rightarrow \frac{I_L}{I_S} = \frac{h_{fe} R_B \cdot R_C}{(R_L + R_C)(R_B + Z_B)}$$



Power gain


- supply voltage

voltage gain

i/p impedance

frequency response
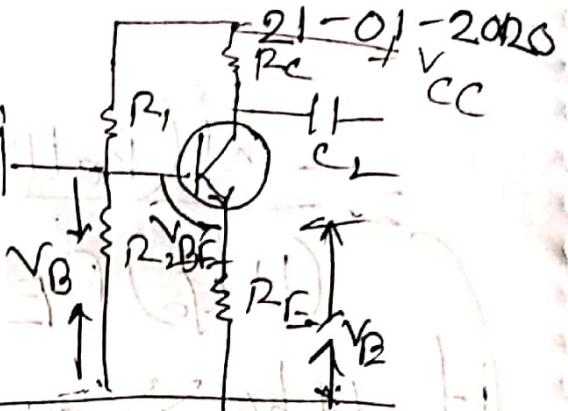
$$A_v = -\frac{h_{fe}(R_e U_{RL})}{a h_{ie}}$$



$$I_C \gg 500 \mu A$$

$$V_{CC} = V_E + V_{CE} + V_{RE}$$

$$I_C \approx I_E$$

$$V_B = V_E + V_{BE}$$

$$\Rightarrow V_E = V_B - V_{BE}$$

$$I_E = \frac{V_E}{R_E}, I_C = \frac{V_{RE}}{R_E}$$

$$V_{RC} = V_{CC} - V_{CE} - V_{RE}$$

for the good biasing stability


$$R_2 = \frac{V_B}{I_2}$$

$$R_1 = \frac{V_{EC} - V_B}{I_1 + I_B}$$

$$V_B = V_{BE} + V_{RE}$$

$$V_B = 3.8 V$$

$$I_2 > \frac{I_C}{10}$$

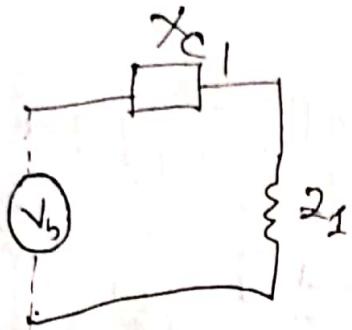

degree of dev

$$= \frac{Z_1}{R_L}$$

$$X_{C_2} > \frac{R_L}{10}$$

Bypass Capacitor

$$X_C = \frac{1}{2\pi f}$$

$$\begin{aligned} A_V &= -\frac{h_{fe}(R_C || R_L)}{h_{ie} + (1+h_{fe})(R_E || X_{C_2})} \\ &= -\frac{h_{fe}(R_C || R_L)}{h_{ie} + (1+h_{fe})X_{C_2}} \\ &= -\frac{h_{fe}(R_C || R_L)}{h_{ie} - j(1+h_{fe})X_{C_2}} \end{aligned}$$

$$\text{let, } h = (1+h_{fe})X_{C_2}$$

$$X_{C_B} = \frac{h_{ie}}{1+h_{fe}}$$

|A\_V|

$$= -\frac{h_{fe}(R_C || R_L)}{f^2 h_{ie} + (1+h_{fe})^2 X_{C_2}}$$

$$\begin{aligned} &\therefore -h_{fe}(R_C || R_L) \approx A_V \\ &\text{and } h_{ie} \approx \sqrt{2} \\ &\Rightarrow |A_V| = \frac{|A_V|}{\sqrt{2}} \end{aligned}$$

## $h$ -parameter

$$h_{ie} = \frac{V_{be}}{I_B}$$

$$h_{ie} = \frac{V_{be}}{I_B / V_{CE}}$$


for reverse bias

$$h_{re} = \frac{\Delta V_{BE}}{\Delta V_{CE} / I_B}$$

for forward bias,

$$h_{fe} = \frac{I_C}{I_B} / r_{ce}$$

common-emitter circuit:

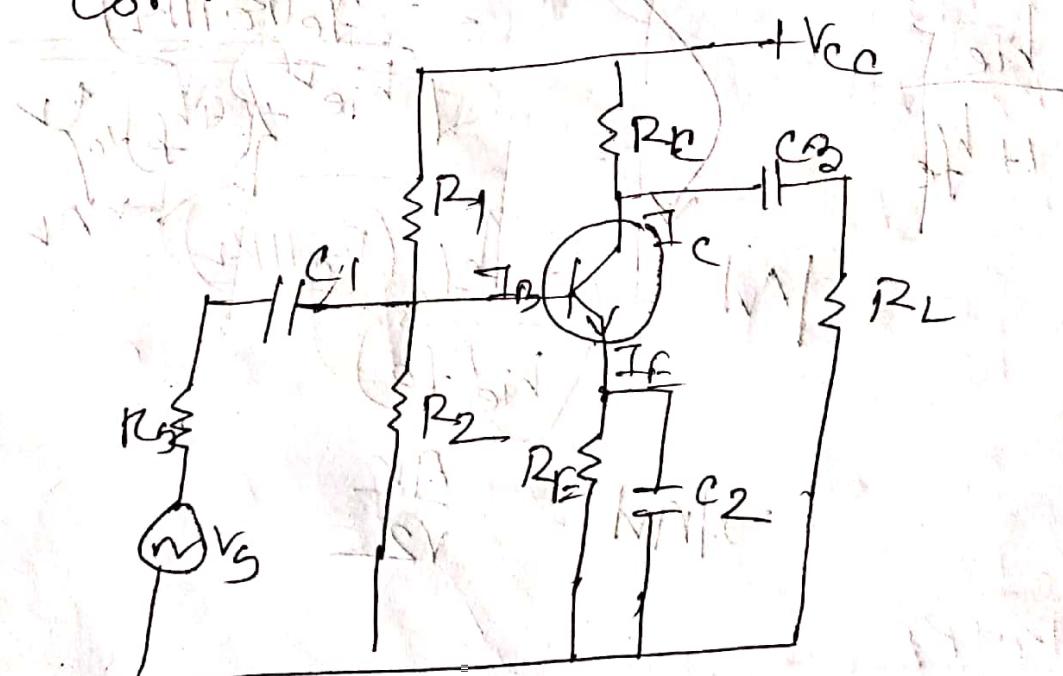

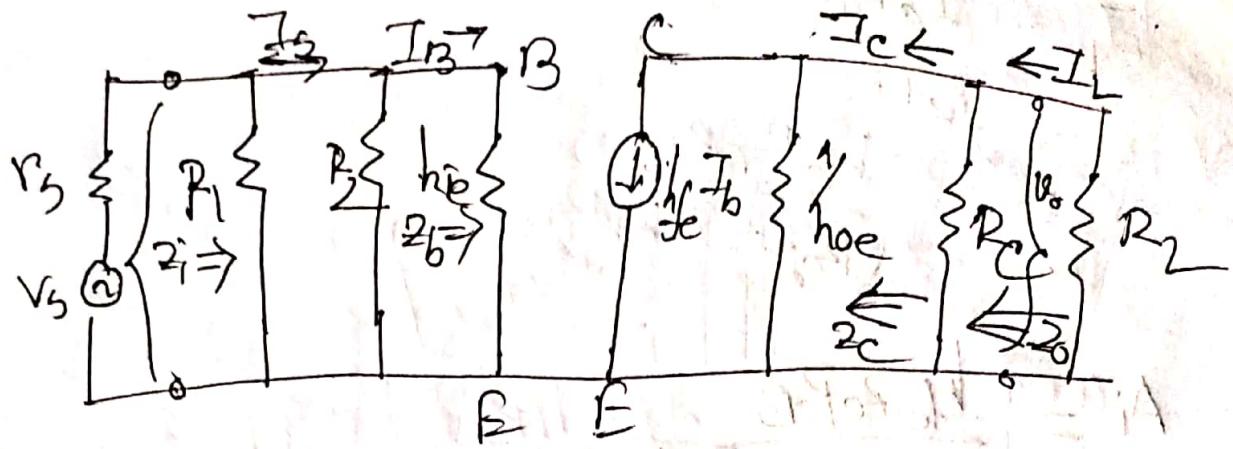


Fig 8-h-parameter equivalent circuit for  
CE circuit, (bypassed capacitor)

input impedance,

$$Z_{in} = R_1 \parallel R_2 \parallel Z_b$$

output impedance:

$$Z_o = R_C \parallel h_{oe}$$

voltage gain

$$A_v = \frac{V_o}{V_i}$$

$$V_i = I_b h_{ie} \text{ and } V_o = -I_c (R_C \parallel R_L)$$

$$A_v = \frac{I_b h_{ie}}{-I_c (R_C \parallel R_L)} \Rightarrow A_v = -\frac{h_{ie} (R_C \parallel R_L)}{h_{ie}}$$

current gain:-

$$h_{fe} = \frac{I_c}{I_b}$$

$$I_b = \frac{I_s R_B}{R_B + Z_b}$$

$$R_B = R_1 \parallel R_2$$

$$I_c = \frac{h_{fe} I_s R_B}{R_B + Z_b}$$

$$\Rightarrow \frac{I_c}{I_s} = \frac{h_{fe} R_B}{R_B + Z_b}$$

$$I_L = \frac{I_c R_o}{R_o + R_L}$$


$$\Rightarrow \frac{I_L}{I_S} = \frac{h_{fe} R_o R_c}{(R_o + R_L)(R_o + h_{fe})}$$


$$A_i = \frac{h_{fe} R_o R_c}{(R_o + R_L)(R_o + h_{fe})}$$

power gain (P)

$$AP = A_i A_o$$

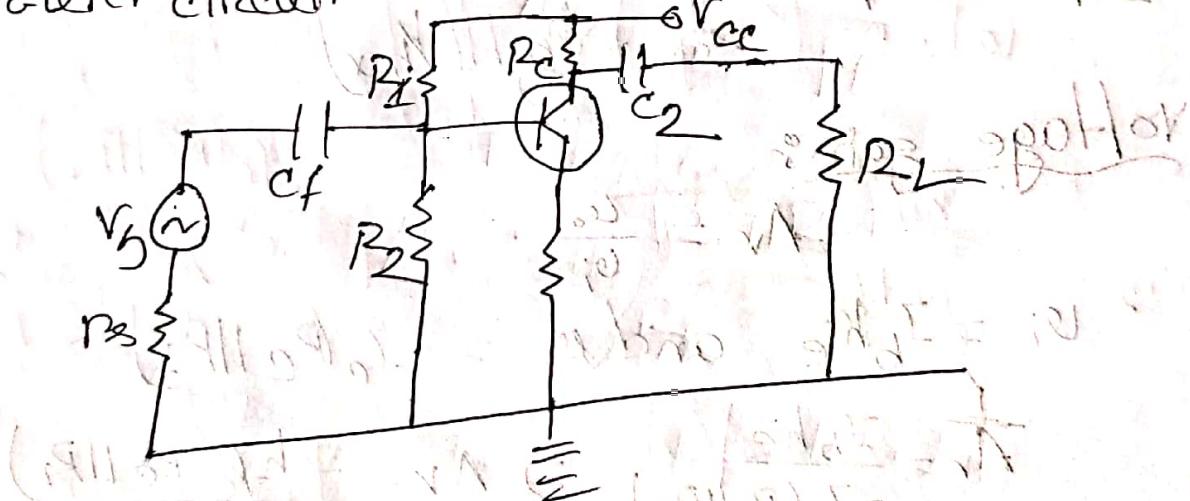Common-emitter configuration with bypassed equivalent circuit.



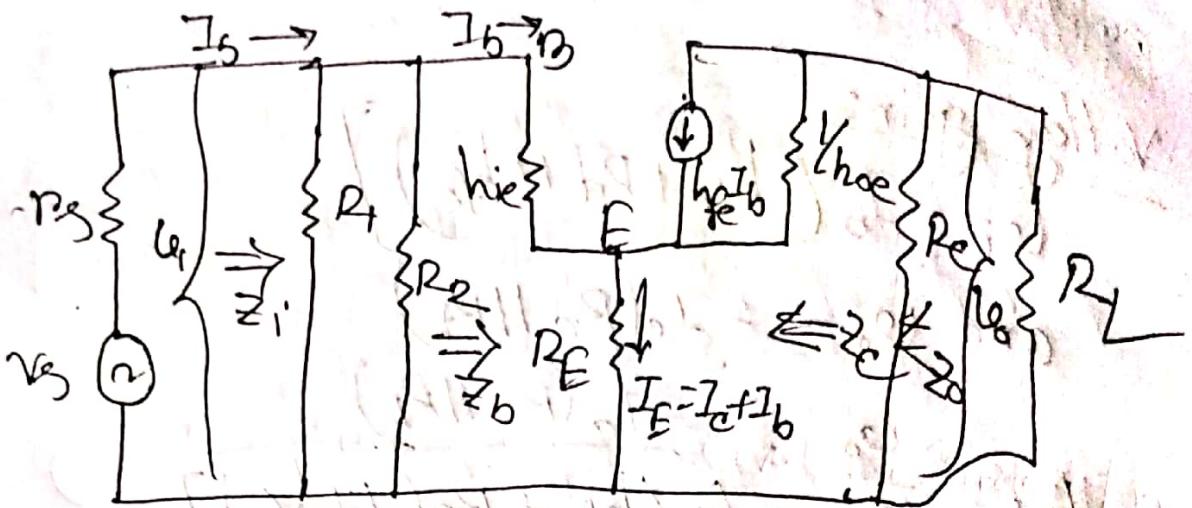

$h$ -parameter equivalent circuit for CE circuit  
with un bypassed emitter circuit.

input impedance:

$$Z_i = I_b h_{ie} + \frac{R_E}{h_{fe}}$$

$$= I_b h_{ie} + R_E (I_b + I_c)$$

$$= I_b h_{ie} + R_E (I_b + h_{fe} I_b)$$

$$= I_b (h_{ie} + R_E (1 + h_{fe}))$$

$$\Rightarrow \frac{Z_i}{I_b} = h_{ie} + R_E (1 + h_{fe})$$

$$\Rightarrow Z_b = h_{ie} + R_E (1 + h_{fe})$$

$$\therefore Z_i = (R_1 H R_2 || R_E) Z_b$$

Output impedances

$$Z_o = R_e$$

Voltage gain

$$V_i = I_b (h_{ie} + R_e (1 + h_{fe}))$$

$$\text{and } V_o = -I_c (R_C || R_L)$$

$$A_v = \frac{V_o}{V_i} = \frac{-I_c (R_C || R_L)}{I_b (h_{ie} + R_e (1 + h_{fe}))}$$



$$= \frac{-h_{fe} (R_C || R_L)}{h_{ie} + R_e (1 + h_{fe})}$$

This reduces to,  $A_v = \frac{(R_C || R_L)}{R_e + R_e}$

$$R_E \gg r_e$$

$$A_v \approx -\frac{(R_C || R_L)}{R_e}$$

## Common-collector circuit

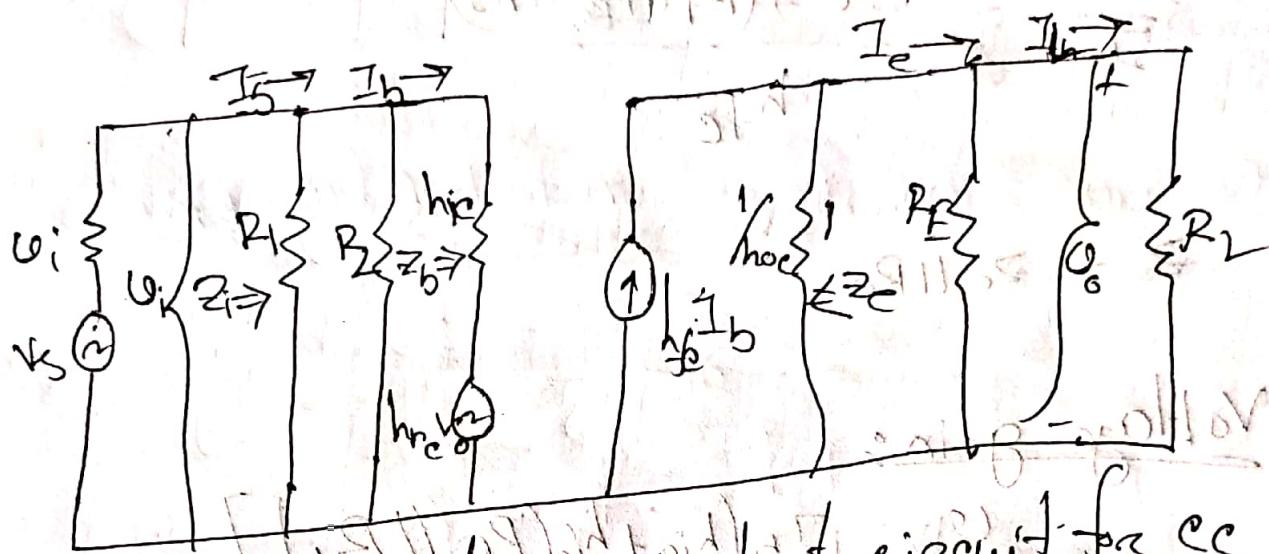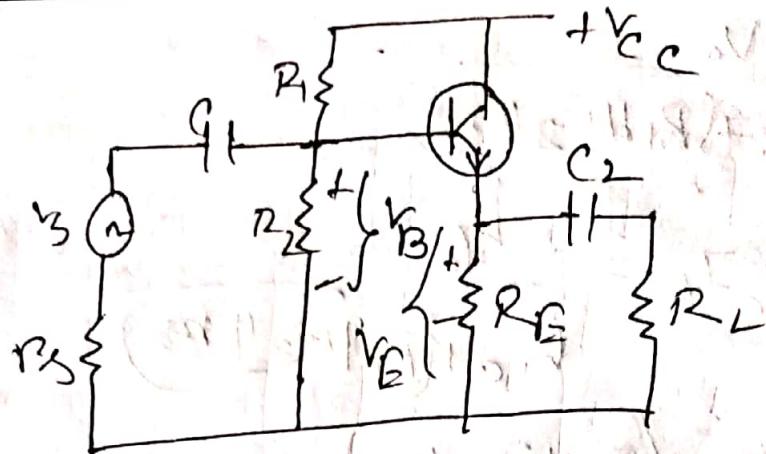

h-parameter equivalent circuit for CC

input impedance

$$V_i = I_b h_{ie} + h_{re}$$

$$= I_b h_{ie} + h_{re} (R_E // R_L)$$

$$= I_b h_{ie} + h_{re} I_b (R_E // R_L)$$

$$\Rightarrow V_i = I_b (h_{ie} + h_{re} (R_E // R_L))$$

$$\Rightarrow \frac{V_i}{I_b} = h_{ie} + h_{re} (R_E // R_L) - z_b - h_{ie} + h_{re} (R_E // R_L)$$

## Output impedances

$$I_b = \frac{V_o}{h_{ic} + (R_1 \parallel R_2 \parallel r_{ds})}$$

$$I_e = h_{fe} I_b = \frac{h_{fe} V_o}{h_{ic} + (R_1 \parallel R_2 \parallel r_{ds})}$$

$$\frac{V_o}{I_e} = \frac{h_{ic} + (R_1 \parallel R_2 \parallel r_{ds})}{h_{fe}}$$

$$Z_o = Z_e \parallel R_L$$

## Voltage gains

$$V_{in} = I_b [h_{ic} + h_{fe} (R_E \parallel R_L)]$$

$$V_o = I_e (R_E \parallel R_L)$$

$$A_v = \frac{V_o}{V_i} = \frac{I_e (R_E \parallel R_L)}{I_b [h_{ic} + h_{fe} (R_E \parallel R_L)]}$$

$$A_O = \frac{(R_E \parallel R_L)}{h_{ib} + (R_E \parallel R_L)}$$

$$A_O \approx 1$$

# Common-base circuit analysis:

internal



27-01-2020

## Introduction to operational analysis:

### operation Amplifier

- high gain

- 2 high i/p impedance terminal

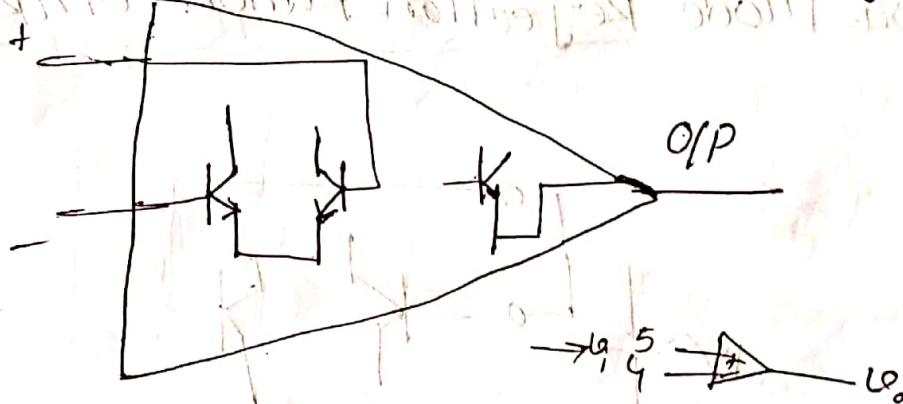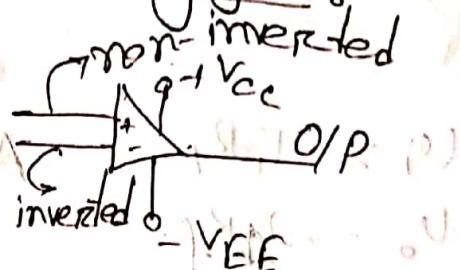


$$\text{Voltage gain} = \frac{V_o}{V_i} = 5 - 4 = 1$$

## Non-inverting amplifiers:


$$\frac{V_o}{R_3} = I_2 R_2$$

$$V_o = I_2 (R_2 + R_3)$$

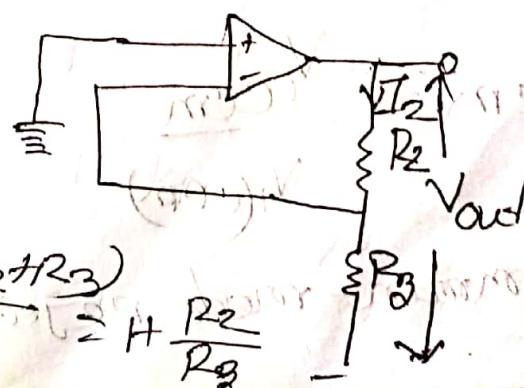
$$A_V = \frac{V_o}{V_i} = \frac{I_2 (R_2 + R_3)}{I_2 R_3} = 1 + \frac{R_2}{R_3}$$



### Inverting amplifier: chapter 8

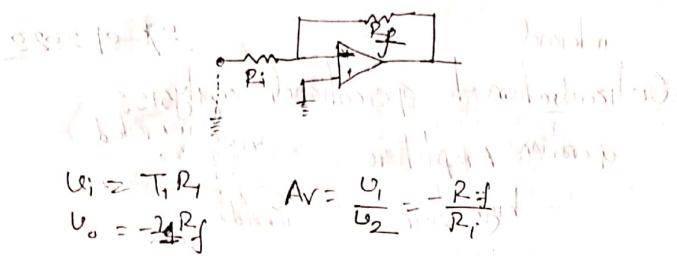

### Common-Mode Rejection Ratio (CMRR)

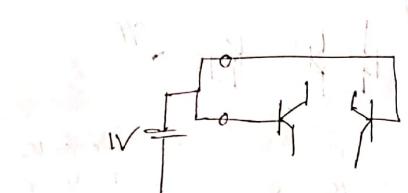

$$\begin{aligned} V_{in} &= V_{1in} - V_{2in} \\ &= 1V - 1V \\ &= 0 \end{aligned}$$


$$A_{cm} = \frac{V_{ocm}}{V_{i(cm)}}$$

$$CMRR = \frac{m}{A_{cm}} = 20 \log \frac{m}{A_{cm}} \text{ dB}$$

# common-mode rejection ratio


### Summing Amplifier

- (i) inverting
- (ii) non-inverting

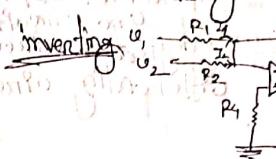

$$\begin{aligned} V_0 &= A_v (V_1 + V_2) \\ I_1 &= \frac{V_1}{R_1} \\ I_2 &= \frac{V_2}{R_2} \\ V_0 &= -(I_1 + I_2) R_3 \\ [R_1 = R_2 = R] &= -\left(\frac{V_1}{R} + \frac{V_2}{R}\right) R_3 \\ V_0 &= -\frac{R_3}{R} (V_1 + V_2) \end{aligned}$$
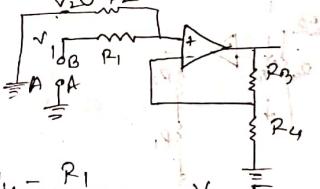
### non-inverting (input-positive from non-inverting)



$$N_{11} = \frac{R_1}{R_1 + R_2}, V_1 = \frac{V_1}{2} [R_1 = R_2], V_2 = 0$$


$$V_{1/2} = \frac{V_1}{2}, V_2 = 0$$

$$\begin{aligned} V_{in} &= V_1 + V_{1/2} \\ &= \frac{V_1 + V_2}{2} \end{aligned}$$

$$V_o = A_v \cdot V_{in}$$

$$= \left( \frac{R_3 + R_4}{R_4} \right) \cdot (V_1 + V_2)$$


### Difference Amplifier:

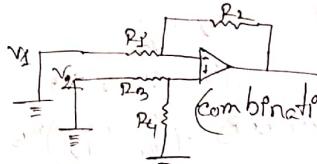

Combining of inverting & non-inverting

$$V_o = V_2 - V_1$$

$$V_{o1} = -\frac{R_2}{R_1} V_1 = -V_1$$

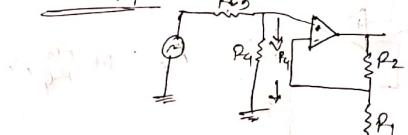

$$V_{o1} = \frac{R_2}{R_3 + R_4} V_2$$

$$V_{o2} = \frac{R_1 + R_2}{R_1} V_{o1}$$

$$V_{o2} = \frac{R_1 + R_2}{R_1} \times \frac{R_2}{R_3 + R_4} V_2$$

$$V_o = V_{o2} - V_{o1}$$

$$\approx V_2 - V_1$$

$$V_o = V_1 + V_2 \quad \text{chap 1 & 2}$$

$$= A_v(V_1 + V_2)$$

h.w Operational amplifier  
and circuit  
integrated circuit  
differentiating circuit


Steko-rate

of digital circuit




Zero crossing-Detector


chapter 2

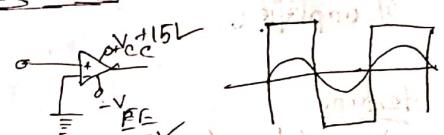

Inverting speed trigger

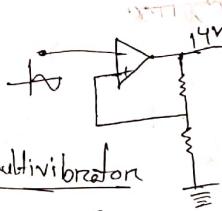

astable-multivibrator

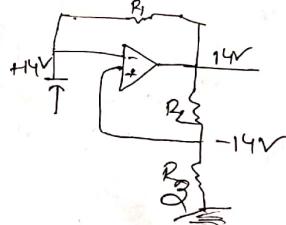


# Uni Junction Transistor(UJT)

## use

- i) oscilloscope make
- ii) amplifier

feature

- i) A stable triggering voltage

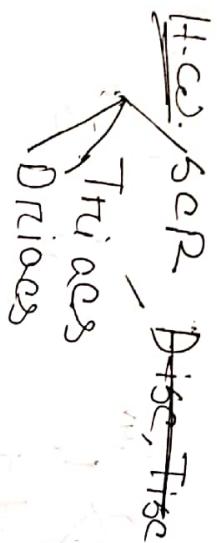

$$\text{dc power} = \text{ac power} + \text{loss}$$

17-02-20

## Transformer couple Transformer:



$$R_L = \frac{V_2}{I_2}$$

$$R_L' = \frac{V_1}{I_1}$$

Basics transformer theory.

$$\frac{V_1}{V_2} = \frac{I_2}{I_1} \quad , \quad \frac{V_1}{V_2} = \frac{N_1}{N_2} = \frac{I_2}{I_1}$$

$$P_1 = P_2 \Rightarrow V_1 I_1 = V_2 I_2$$

$$\Rightarrow I_1 = \frac{N_2}{N_1} I_2$$

$$R_L' = \frac{V_1}{I_1}$$

$$= \frac{(N_2)^2 R_L}{n^2 N_1^2}$$

Efficiency of a class A power

$$\eta = \frac{\text{ac o/p power}}{\text{input power}} \times 100\%$$

$$P_i = v_{ce} E \times I_{avg}$$


$$P_o = V_{Dmax} \times I_{rms}$$




class B power amplifier

25 - 50% maximum efficiency



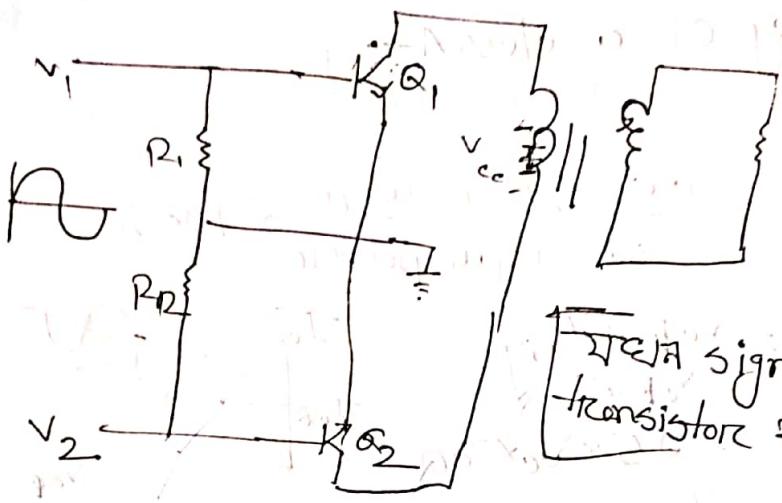

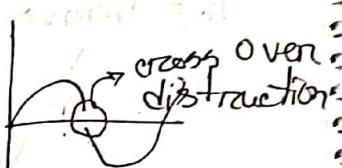যদি signal পার রয়েন  
transistor শক্তিক্ষমতা,



# cross over distortion

# spliter (use Transformer) মাঝে বিভাজন

